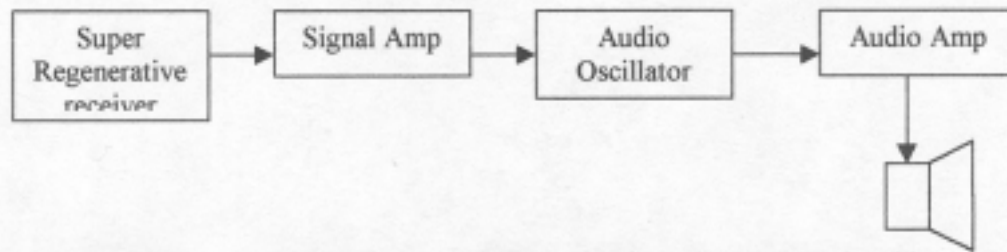


##### 5- Receiver block diagram and circuit description



The super regenerative receiver recovers the 600Hz pulse from the RF. The signal is amplified and rectified to trigger the audio oscillator to produce an ultrasonic tone which is then amplified and sent to the speaker.